

Problemas propuestos de algebra Booleana y puer. lógicas (4)

4.1 Funciones  $+$  y  $\cdot$  asociativas. Comprobarlo con la T.V.

$$S = a + b + c \Rightarrow S = (a + b) + c$$

| a | b | c | S |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

| a | b | S' = a + b |
|---|---|------------|
| 0 | 0 | 0          |
| 0 | 1 | 1          |
| 1 | 0 | 1          |
| 1 | 1 | 1          |

| S' | c | S = (a+b)+c |
|----|---|-------------|
| 0  | 0 | 0           |
| 0  | 1 | 1           |
| 1  | 0 | 1           |
| 1  | 1 | 1           |

Si "a" y "b" y "c" son  $\emptyset \Rightarrow$

salida =  $\emptyset$

4.2 Aplicar teorema de Shannon a la expresion  $\overline{a+b \cdot c}$  y comprobar la igualdad con k T.V.

$$S = \overline{a + b \cdot c} \xrightarrow{\text{Morgan}} S = \overline{a} \cdot \overline{b \cdot c} \xrightarrow{\text{Morgan}} \overline{a} \cdot (\overline{b} + \overline{c}) \xrightarrow{\text{distrib}} \overline{a} \overline{b} + \overline{a} \overline{c}$$

$$\text{Shannon} \rightarrow S = \overline{a} \overline{b} + \overline{a} \overline{c} = \overline{a} \overline{b} (c + \overline{c}) + \overline{a} \overline{c} (b + \overline{b}) =$$

$$S = \underbrace{\overline{a} \overline{b} \overline{c}}_{m_0} + \underbrace{\overline{a} \overline{b} c}_{m_1} + \underbrace{\overline{a} b \overline{c}}_{m_3} + \underbrace{\overline{a} b c}_{m_2}$$

| a | b | c | S (canónica) | S = a + b $\overline{c}$ |
|---|---|---|--------------|--------------------------|
| 0 | 0 | 0 | 1            | 1                        |
| 0 | 0 | 1 | 1            | 1                        |
| 0 | 1 | 0 | 0            | 0                        |
| 0 | 1 | 1 | 1            | 1                        |
| 1 | 0 | 0 | 0            | 0                        |
| 1 | 0 | 1 | 0            | 0                        |
| 1 | 1 | 0 | 0            | 0                        |
| 1 | 1 | 1 | 0            | 0                        |

Si a =  $\emptyset$  y b = 1 y c =  $\emptyset$   
entonces  $a + b \overline{c} = 1 \Rightarrow S = 0$ .  
Resto S = 1

En S si a = 1  $\Rightarrow S = 0$

4.3 Teorema de la expansión

$$S = abc + a\bar{b}c + \bar{a}bc = a(\bar{b}c + bc) + \bar{a}(bc)$$

4.4 Logigrama

|   | c | b | a | F |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 0 | x |
| 3 | 0 | 1 | 1 | 1 |
| 4 | 1 | 0 | 0 | 0 |
| 5 | 1 | 0 | 1 | x |
| 6 | 1 | 1 | 0 | 1 |
| 7 | 1 | 1 | 1 | 1 |

$$F = \sum (m_1, m_3, m_6, m_7) + x(2, 5)$$

|           | $\bar{c}$      |                | c              |                |
|-----------|----------------|----------------|----------------|----------------|
|           | $\bar{b}$      | b              | b              | $\bar{b}$      |
| $\bar{a}$ | m <sub>0</sub> | m <sub>2</sub> | m <sub>6</sub> | m <sub>4</sub> |
| a         | m <sub>1</sub> | m <sub>3</sub> | m <sub>7</sub> | m <sub>5</sub> |

|           | $\bar{c}$ |   | c |           |
|-----------|-----------|---|---|-----------|
|           | $\bar{b}$ | b | b | $\bar{b}$ |
| $\bar{a}$ |           | x | 1 |           |
| a         | 1         | 1 | 1 | x         |

1 → a  
2 → b

$$F = a + b$$



4.5 TV y logigrama de  $f(c, b, a) = \sum (0, 6, 7) + x(1, 2, 5)$

|   | c | b | a | F |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | x |
| 2 | 0 | 1 | 0 | x |
| 3 | 0 | 1 | 1 | 0 |
| 4 | 1 | 0 | 0 | 0 |
| 5 | 1 | 0 | 1 | x |
| 6 | 1 | 1 | 0 | 1 |
| 7 | 1 | 1 | 1 | 1 |

|           | $\bar{c}$ |   | c |           |
|-----------|-----------|---|---|-----------|
|           | $\bar{b}$ | b | b | $\bar{b}$ |
| $\bar{a}$ | 1         | x | 1 |           |
| a         | x         |   | 1 | x         |


1 → bc  
2 →  $\bar{b}\bar{c}$

$$F = bc + \bar{b}\bar{c} \Rightarrow F = \overline{b \oplus c}$$



4.6) TV y circuito lógico de  $f(c,b,a) = \prod(3,4) \cdot x(2,5,6)$



| $\overline{B}$ | $\overline{A}$ | c | b | a | F |
|----------------|----------------|---|---|---|---|
| 0              | 7              | 0 | 0 | 0 | 1 |
| 1              | 6              | 0 | 0 | 1 | x |
| 2              | 5              | 0 | 1 | 0 | x |
| 3              | 4              | 0 | 1 | 1 | 0 |
| 4              | 3              | 1 | 0 | 0 | 0 |
| 5              | 2              | 1 | 0 | 1 | x |
| 6              | 1              | 1 | 1 | 0 | 1 |
| 7              | 0              | 1 | 1 | 1 | 1 |

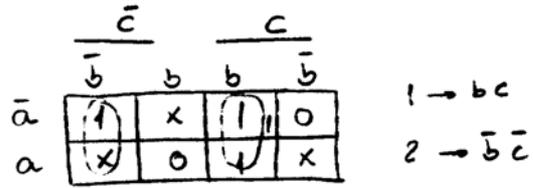


$$F = bc + \overline{b}\overline{c} \Rightarrow F = b \oplus c$$



4.7) Cronograma de una AND de 4 entradas

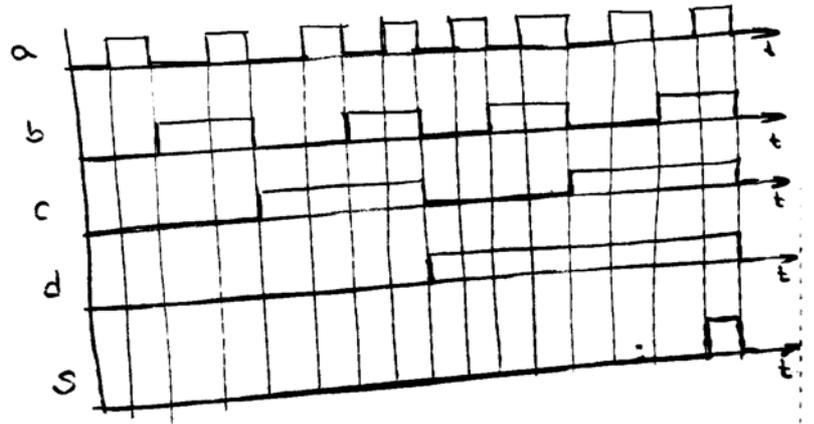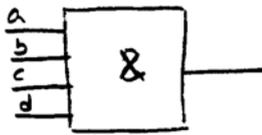

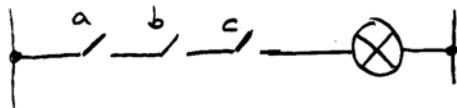4.8) Circuito eléctrico AND con 3 interruptores




4.9) Logigrama para una alarma que active una sirena (s) cuando está activada la señal a y se produzca la rotura de un cristal (b)

| a | b | S |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

$$S = a \cdot b$$




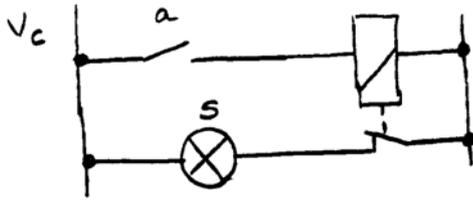4.11) Circuito eléctrico con relés para la función NOT



4.16) Diseñar un generador de paridad par para 4 bits

| a | b | c | d | P |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 |

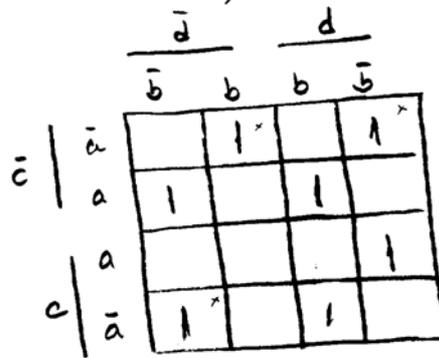

3 bits  $\Rightarrow f(b,c,d) = \bar{b}\bar{c}d + \bar{b}c\bar{d} + b\bar{c}\bar{d} + bcd$

$$f(b,c,d) = \bar{b}(\bar{c}d + c\bar{d}) + b(\bar{c}\bar{d} + cd) =$$

$$f(b,c,d) = \bar{b}(c \oplus d) + b(\overline{c \oplus d}) =$$

$$f(b,c,d) = b \oplus (c \oplus d)$$


4 bits Para  $a=0 \Rightarrow f(b,c,d)$

"  $a=1 \Rightarrow \overline{f(b,c,d)}$

Si  $f(b,c,d) = m \Rightarrow$

$$f(a,b,c,d) = \bar{a}m + a\bar{m} = a \oplus m \Rightarrow P = a \oplus (b \oplus (c \oplus d))$$

$$P = a \oplus (b \oplus (c \oplus d))$$

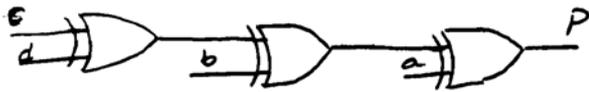

4.15 Generador de paridad de 8 bit

De acuerdo al razonamiento de 4.14 =

$$P = a \oplus (b \oplus (c \oplus (d \oplus (e \oplus (f \oplus (g \oplus h))))))$$



Problemas resueltos Gestión (Alg. Boole)

④ ① Minterm L1 según TV

$$L1 = m_0 + m_1 + m_2 + m_3 + m_4 + m_5 + m_6 \Rightarrow b$$

② Minterm L2 según TV

$$L2 = m_3 + m_4 + m_5 + m_6 + m_7 + m_8 + m_9 + m_{10} + m_{11} + m_{12} \Rightarrow \bar{d}$$

③ Minterm L3 según TV

$$L3 = m_9 + m_{10} + m_{11} + m_{12} + m_{13} + m_{14} + m_{15} \Rightarrow a$$

|           |           | $\bar{a}$ |       | $a$      |           |
|-----------|-----------|-----------|-------|----------|-----------|
|           |           | $\bar{c}$ | $c$   | $c$      | $\bar{c}$ |
| $\bar{b}$ | $\bar{d}$ | $m_0$     | $m_2$ | $m_{10}$ | $m_8$     |
|           | $d$       | $m_1$     | $m_3$ | $m_{11}$ | $m_9$     |
| $b$       | $d$       | $m_5$     | $m_7$ | $m_{15}$ | $m_{13}$  |
|           | $\bar{d}$ | $m_4$     | $m_6$ | $m_{14}$ | $m_{12}$  |

**L1**

|           |           | $\bar{a}$ |     | $a$ |           |
|-----------|-----------|-----------|-----|-----|-----------|
|           |           | $\bar{c}$ | $c$ | $c$ | $\bar{c}$ |
| $\bar{b}$ | $\bar{d}$ | 1         | 1   | 0   | 0         |
|           | $d$       | 1         | 1   | 0   | 0         |
| $b$       | $d$       | 1         | 0   | 0   | 0         |
|           | $\bar{d}$ | 1         | 1   | 0   | 0         |

**L2**

|           |           | $\bar{a}$ |     | $a$ |           |
|-----------|-----------|-----------|-----|-----|-----------|
|           |           | $\bar{c}$ | $c$ | $c$ | $\bar{c}$ |
| $\bar{b}$ | $\bar{d}$ | 0         | 0   | 1   | 1         |
|           | $d$       | 0         | 1   | 1   | 1         |
| $b$       | $d$       | 1         | 1   | 0   | 0         |
|           | $\bar{d}$ | 1         | 1   | 0   | 1         |

$$L1 = \bar{a}\bar{c} + \bar{a}b + \bar{a}\bar{d}$$

$$L1 = \bar{a}(\bar{c} + b + \bar{d}) \Rightarrow \underline{\underline{b}}$$

④


**L3**

|           |           | $\bar{a}$ |     | $a$ |           |
|-----------|-----------|-----------|-----|-----|-----------|
|           |           | $\bar{c}$ | $c$ | $c$ | $\bar{c}$ |
| $\bar{b}$ | $\bar{d}$ | 0         | 0   | 1   | 0         |
|           | $d$       | 0         | 0   | 1   | 1         |
| $b$       | $d$       | 0         | 0   | 1   | 1         |
|           | $\bar{d}$ | 0         | 0   | 1   | 1         |

⑤  $L2 = \bar{a}b + a\bar{b} + \bar{a}cd + b\bar{c}\bar{d}$

⑦  $L1 = \bar{a}(\bar{c} + \bar{b} + \bar{d}) =$

$$L1 = \bar{a}(c \cdot b \cdot d)$$

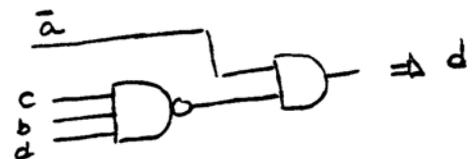

⑥  $L3 = ac + ad + ab = a(b + c + d)$

## Funciones lógicas

$$\textcircled{1} F = \overline{(\overline{a+b})c + \bar{a} + \bar{b}d + \bar{c}\bar{d}} = \overline{\overline{a+b}c} \cdot \overline{\bar{a}} \cdot \overline{\bar{b}d} \cdot \overline{\bar{c}\bar{d}} =$$
$$F = ((a+b) + \bar{c}) \cdot a \cdot (b + \bar{d}) \cdot (c+d) \Rightarrow a$$

$$\textcircled{2} \text{ La función de NOR exclusiva si 0 exclusiva: } a\bar{b} + \bar{a}b$$
$$\text{Nor exclu} = \overline{a\bar{b} + \bar{a}b} = \overline{a\bar{b}} \cdot \overline{\bar{a}b} = (\bar{a} + b)(a + \bar{b}) =$$
$$= \frac{\bar{a}a}{0} + \bar{a}\bar{b} + ab + \frac{b\bar{b}}{0} = \bar{a}\bar{b} + ab \Rightarrow \underline{c}$$

$$\textcircled{3} f(a, b, c, d, e) = (ab + \bar{c})(\bar{d} + e + b\bar{a}) \quad \text{¿ } f(a, b, c, d, e) ?$$
$$\overline{f(a, b, c, d, e)} = \overline{(ab + \bar{c})(\bar{d} + e + b\bar{a})} = \overline{ab + \bar{c}} + \overline{\bar{d} + e + b\bar{a}} =$$
$$= (\overline{ab} \cdot c) + [(\bar{d} + e) \cdot \overline{b\bar{a}}] = [(\bar{a} + \bar{b})c] + [(\bar{d} + e) \cdot (b + a)]$$

$\Downarrow$   
b

$$\textcircled{4} \text{ Simplificar } f(a, b, c) = (a+b)(a+c)(b+c) =$$

$$f(a, b, c) = \underbrace{(aa + ac + ab + bc)}_a (b+c) = (a + bc)(b+c) =$$
$$\underbrace{a(1+c+b)}_a$$

$$f(a, b, c) = ab + ac + \underbrace{bbc}_{bc} + \underbrace{bcc}_{bc} = ab + ac + bc$$

si revés

$$a) \underline{a+c} + \underline{ac} + b+c = a+b+c \Rightarrow \text{No}$$

$$b) (b+c)(a+bc) = ba + bbc + ac + bcc = ab + ac + bc \Rightarrow \underline{SI}$$

$$\textcircled{5} \quad f(a, b, c, d, e) = (\bar{a} \cdot \bar{b} + d)(\bar{b} + e) + c\bar{d} \quad \text{para } a=c=e=0 \text{ y } b=d=1 \text{ es}$$

$$f(a, b, c, d, e) = (1 \cdot 0 + 1)(0 + 0) + 0 \cdot 0 = 0 \Rightarrow \underline{a}$$

$$\textcircled{6} \quad f(a, b, c) = ab + \bar{b} = (a + \bar{b})(b + \bar{b}) = a + \bar{b} \Rightarrow \underline{b}$$

$$\textcircled{7} \quad f(a, b, c) = \bar{a} + \bar{c} =$$

$$\begin{aligned} b) \quad f(a, b, c) &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + \bar{a}b\bar{c} + a\bar{b}c + \bar{a} + \bar{c} + abc \\ &= \bar{a}(1 + \bar{b}\bar{c} + \bar{b}c + b\bar{c}) + \bar{c}(1 + ab + a\bar{b}) + abc = \\ &= \bar{a} + \bar{c} + abc \Rightarrow \text{No} \end{aligned}$$

$$\begin{aligned} d) \quad f(a, b, c) &= \bar{a} + \bar{a}\bar{b}\bar{c} + ab\bar{c} = \bar{a} + a\bar{c}(b + \bar{b}) = \bar{a} + a\bar{c} = \\ &= (\bar{a} + a)(\bar{a} + \bar{c}) = \bar{a} + \bar{c} \Rightarrow \underline{51} \end{aligned}$$

### Simplificación de funciones

$$\textcircled{1} \quad f(a, b) = \overline{a + a\bar{b}} = \overline{a(1 + \bar{b})} = \bar{a} = \bar{a}b + \bar{a}\bar{b} = m_1 + m_0$$

$$\textcircled{2} \quad f(a, b) = \overline{a + a\bar{b}} = m_1 + m_0 =$$

$$\overline{f(a, b)} = m_2 + m_3 \Rightarrow f(a, b) = \overline{m_2 + m_3} = \overline{m_2} \cdot \overline{m_3} = M_1 + M_0 \Rightarrow \underline{d}$$

$$\begin{aligned} \textcircled{3} \quad f(a, b) &= \overline{\bar{a}(b + \bar{a}\bar{b})} = \overline{\bar{a}(b + \bar{a})(b + \bar{b})} = \overline{\bar{a}(b + \bar{a})} = \\ &= \overline{\bar{a}b + \bar{a}\bar{a}} = \overline{\bar{a}(1 + b)} = \bar{a} = \bar{a}b + a\bar{b} = m_3 + m_2 \end{aligned}$$

$$\overline{f(a, b)} = m_0 + m_1 \Rightarrow f(a, b) = \overline{m_0 + m_1} = \overline{m_0} \cdot \overline{m_1} = M_3 \cdot M_2$$

$$f(a, b) = \Pi(2, 3) \Rightarrow b$$

$$\textcircled{4} \quad f(a,b) = \overline{\bar{a}(b+\bar{a}\bar{b})} \cdot \overline{\bar{a}(\bar{a}+b)(b+\bar{b})} = \overline{\bar{a}(\bar{a}+b)} =$$

$$= \overline{\bar{a}\bar{a} + \bar{a}b} = \overline{\bar{a}(1+b)} = a = ab + a\bar{b} = m_2 + m_3$$

$$f(a,b) = \Sigma(2,3) \Rightarrow \underline{b}$$

$$\textcircled{5} \quad f(a,b) = \overline{(\bar{a} + a\bar{b})} = \overline{(\bar{a}+a)(\bar{a}+\bar{b})} = \overline{\bar{a}+\bar{b}} = ab = m_3$$

$$f(a,b) = \Sigma(3) \Rightarrow \underline{c}$$

$$\textcircled{6} \quad f(a,b) = \overline{\bar{a} + a\bar{b}} = m_3 \Rightarrow f(a,b) = m_0 + m_1 + m_2 \Rightarrow$$

$$f(a,b) = \overline{m_0 + m_1 + m_2} = \overline{m_0} \cdot \overline{m_1} \cdot \overline{m_2} = M_3 \cdot M_2 \cdot M_1$$

$$f(a,b) = \Pi(1,2,3) \Rightarrow \underline{a}$$

$$\textcircled{7} \quad f_1(a,b) = \Sigma(0,3)$$

$$f_2(c,d) = \Pi(1,2)$$

$$g(a,b,c,d) = f_1(a,b) \oplus f_2(c,d)$$

$$f_1 = m_0 + m_3 = \bar{a}\bar{b} + ab$$

$$f_2 = M_1 \cdot M_2 \Rightarrow \bar{f}_2 = M_0 + M_3 \Rightarrow f_2 = \overline{M_0 + M_3} = \overline{M_0} \cdot \overline{M_3}$$

$$f_2 = m_3 \cdot m_0 = cd + \bar{c}\bar{d}$$

$$g = (\bar{a}\bar{b} + ab) \oplus (cd + \bar{c}\bar{d}) = (\bar{a}\bar{b} + ab)(cd + \bar{c}\bar{d}) + (\bar{a}\bar{b} + ab)(\bar{c}d + c\bar{d})$$

$$= (\overline{\bar{a}\bar{b}} \cdot \overline{ab})(cd + \bar{c}\bar{d}) + (\bar{a}\bar{b} + ab)(\bar{c}\bar{d} + c\bar{c}\bar{d}) =$$

$$= (a+b)(\bar{a}+\bar{b})(cd + \bar{c}\bar{d}) + (\bar{a}\bar{b} + ab)(\bar{c}+\bar{d})(c+d) =$$

$$= (\overline{a\bar{a}} + \overline{a\bar{b}} + \overline{\bar{a}b} + \overline{b\bar{b}})(cd + \bar{c}\bar{d}) + (\overline{c\bar{c}} + \overline{\bar{c}d} + \overline{c\bar{d}} + \overline{d\bar{d}})(\bar{a}\bar{b} + ab) =$$

$$= \underbrace{a\bar{b}cd}_{m_{11}} + \underbrace{a\bar{b}\bar{c}\bar{d}}_{m_8} + \underbrace{\bar{a}bcd}_{m_7} + \underbrace{\bar{a}\bar{b}c\bar{d}}_{m_4} + \underbrace{\bar{a}\bar{b}\bar{c}d}_{m_1} + \underbrace{ab\bar{c}\bar{d}}_{m_{13}} + \underbrace{ab\bar{c}d}_{m_{14}}$$

$$g = \Pi(1,2,4,7,8,11,13,14) \Rightarrow \underline{c}$$

8)  $A = (a_1, a_0) \times B = (b_1, b_0) \Rightarrow P(p_3, p_2, p_1, p_0)$

| $a_1$ | $a_0$ | $b_1$ | $b_0$ | $p_3$ | $p_2$ | $p_1$ | $p_0$ |
|-------|-------|-------|-------|-------|-------|-------|-------|
| 0     | 0     | 0     | 0     | 0     | 0     | 0     | 0     |
| 0     | 0     | 0     | 1     | 0     | 0     | 0     | 0     |
| 0     | 0     | 1     | 0     | 0     | 0     | 0     | 0     |
| 0     | 0     | 1     | 1     | 0     | 0     | 0     | 0     |
| 0     | 1     | 0     | 0     | 0     | 0     | 0     | 0     |
| 0     | 1     | 0     | 1     | 0     | 0     | 0     | 1     |
| 0     | 1     | 1     | 0     | 0     | 0     | 1     | 0     |
| 0     | 1     | 1     | 1     | 0     | 0     | 1     | 1     |
| 1     | 0     | 0     | 0     | 0     | 0     | 0     | 0     |
| 1     | 0     | 0     | 1     | 0     | 0     | 1     | 0     |
| 1     | 0     | 1     | 0     | 0     | 1     | 0     | 0     |
| 1     | 0     | 1     | 1     | 0     | 1     | 1     | 0     |
| 1     | 1     | 0     | 0     | 0     | 0     | 0     | 0     |
| 1     | 1     | 0     | 1     | 0     | 0     | 1     | 1     |
| 1     | 1     | 1     | 0     | 0     | 1     | 1     | 0     |
| 1     | 1     | 1     | 1     | 1     | 0     | 0     | 1     |

$p_3 = 1 \Leftrightarrow A \times B > 8$   
 $\Downarrow$   
 $A = 3 \quad B = 3 \quad \left. \begin{array}{l} \\ \end{array} \right\} 9$

$p_3 = \sum (15) \Rightarrow \underline{\underline{d}}$

9) Problema 8 sacar función canónica de  $p_1$

$p_1 = \sum (6, 7, 9, 11, 13, 14) \Rightarrow \underline{\underline{a}}$

10) Problema 8 sacar función canónica de  $p_0$

$p_0 = \sum (5, 7, 13, 15) \Rightarrow \underline{\underline{c}}$

11) Problema 8 fun. can.  $p_2$

$p_2 = \sum (10, 11, 14) \Rightarrow \underline{\underline{d}}$